

THE UNITED REPUBLIC OF TANZANIA NATIONAL EXAMINATIONS COUNCIL CERTIFICATE OF SECONDARY EDUCATION EXAMINATION

083

ELECTRONICS AND RADIO REPAIR

(For Both School and Private Candidates)

TIME: 3 Hours

16 November 2000 P.M.

Instructions

- 1. This paper consists of sections A and B.
- 2. There are SEVEN (7) questions in section A and FIVE (5) questions in section B.
- 3. Attempt TEN (10) questions, SIX (6) questions from section A and FOUR (4) questions from section B
- 4. Write your Examination Number on every page of your answer bookfet(s).

This paper consists of 4 printed pages

0083

SECTION A

- 1. (a) Explain what is meant by the term free electrons.
 - (b) Explain the behaviour of free electrons in presence of an electric field.
 - (c) Mention the two types of current flow through a semi-conductor crystal under the influence of an electric field.
 - (d) List two common types of donor and acceptor impurities.
- (a) Mention two types of bi-polar transistors.
 - (b) Name three electrodes of the transistor.
 - (c) A transistor exhibits a change of 0.995 mA in its collector current for a change of 1 mA in emitter current. Calculate
 - (i) the common base short-circuit current gain (a).
 - (ii) the common-emitter short circuit current gain (β).
- (a) The meter scale has 30 divisions. What is the current measured by the milliammeter if the number of divisions indicated on the milliammeter is
 - (i) 18 divisions for 3 mA range
 - (ii) 21 divisions for 10 mA range
 - (iii) 27 divisions for 50 mA range?
 - (b) A milliammeter with a meter resistance of 50 ohms and full-scale deflection current of 1 mA has its range of 3 mA and 10 mA. Calculate
 - (i) shunt resistance on each range
 - (ii) input resistance on each range.
- A moving coil meter has full-scale deflection current (Ifs) of 10 mA and has a resistance of 10 ohms.
 The instrument is connected in series with 490 ohm resistor and gives a deflection of half-full scale when connected across a battery.
 - (a) Draw the ohmmeter circuit.
 - (b) Find the c.m.f. of the battery.
 - (c) What is the percentage deflection of the pointer on the scale for supply voltage of 4 V?
- 5. (a) Name five types of capacitors.
 - (b) Two capacitors having capacitance of 10 μF are connected in series across a 200 volt d.c supply. Calculate
 - (i) the charge on each capacitor
 - (ii) the p.d. across each capacitor.



- A tuned circuit is required to cover the frequency range 3.7 MHz to 7.0 MHz. The capacitor is variable and the minimum value of circuit capacitance is 50 pF.
 - (a) What is the required value of inductance?
 - (b) What is the required maximum value of capacitance?
- (a) What is the difference between power and energy? Give one unit of each as used in Electrical Engineering.
 - (b) An electric bulb is rated at 200 V, 75 W. Calculate
 - (i) the current when the bulb is used on 200 V supply.
 - (ii) the cost of running the lamp for 500 hours, if electric energy costs Tshs 10 per kilowatt hour.

SECTION B

- (a) Draw a block diagram of the frequency modulated transmitter. Label each stage and show the signal waveform at each stage.
 - (b) State two advantages of frequency modulation (F.M.) as compared with amplitude modulation (A.M) transmission.
- 9. (a) Explain the term "television"
 - (b) A picture has 400 horizontal and 300 vertical picture elements. Calculate the total number of details in the picture.
- 10. (a) Give the speed of television waves in free air.
 - (b) A television antenna must be equal to half the wavelength of the signal received. Calculate the length of antenna when the television receiver is tuned to a television station transmitting at 300 MHz.
- In accordance with the Tanzania television system, fill in the missing word or number in the following statements.
 - (a) Picture frames are repeated at the rate of ----- per second.
 - (b) The number of scanning lines is ----- per frame.
 - (c) The television channel bandwidth is ----- MHz.
 - (d) Light is connected to video signal by the -----

0083

WE



 The block diagram in Fig. 1 is of a television broadcasting system. The numbered items and blocks represent stages of the system. Write what each block (item) stands for.

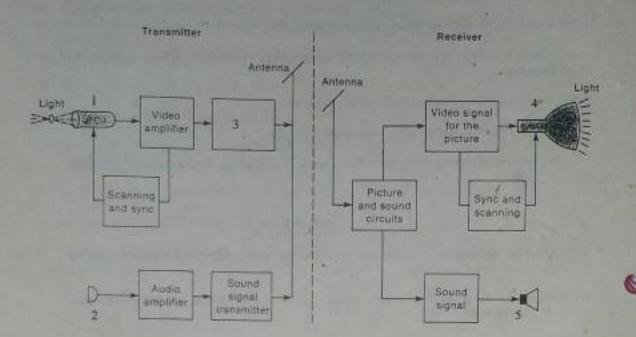


Fig. 1

948