

**THE UNITED REPUBLIC OF TANZANIA  
NATIONAL EXAMINATIONS COUNCIL  
CERTIFICATE OF SECONDARY EDUCATION EXAMINATION**

083

**RADIO AND TELEVISION SERVICING  
(For Both School and Private Candidates)**

Time: 3 Hours

Friday November 12, 2004 p.m.

*Instructions*

1. This paper consists of sections A, B and C.
2. Answer all questions in sections A and B and three (3) questions from section C.
3. Electronic calculators are not allowed in the examination room.
4. Cellular phones are not allowed in the examination room.
5. Write your Examination Number on every page of your answer booklet(s).

*This paper consists of 4 printed pages*



### SECTION A (10 marks)

Answer all questions in this section.

1. For each of the items (i) - (x) choose the correct answer from among the given alternatives and write its letter beside the item number.
- (i) Arsenic, antimony, and phosphorus are all
- A pentavalent
  - B tetravalent
  - C trivalent
  - D acceptor
  - E heavy electron in their orbits.
- (ii) The relationship between  $\alpha$  and  $\beta$  is given by
- A  $\beta = \frac{\alpha}{1 + \alpha}$
  - B  $\beta = \alpha(1 - \alpha)$
  - C  $\alpha = \frac{\beta}{1 + \beta}$
  - D  $\alpha = 1 + \beta$
  - E  $\beta = \frac{\beta - \alpha}{\beta}$
- (iii)  $A_V$  is called the
- A loop gain
  - B gain with feedback
  - C feedback factor
  - D gain without feedback
  - E power gain.
- (iv) The function of a diode is
- A to activate signals
  - B to convert the a.c. to d.c. to the large input waveform
  - C for rectification
  - D to store electric energy
  - E to control the flow of current.
- (v) A full-wave, bi-phase rectifier employs a transformer whose secondary is 300-0-300 V r.m.s. If the circuit is feeding a load resistance of 135 k $\Omega$  the average output current is
- A 2 mA
  - B 1 mA
  - C 1.414 mA
  - D 2.828 mA
  - E 10 mA.
- (vi) Magnetic deflection is used in TV picture tubes
- A because the coils occupy less space than the plates used for electrostatic
  - B to make possible the very wide angle deflection required
  - C because of the high scanning frequency
  - D because better picture quality is possible
  - E because of the simplicity of the method.



- (vii) Micro-farad is a unit of
- A power
  - B capacitance
  - C voltage
  - D charge
  - E resistance.
- (viii) The device which controls the flow of current is called
- A current
  - B resistor
  - C capacitor
  - D inductor
  - E zenner.
- (ix) An oscillator is
- A a tuned amplifier whereby some of the output energy is fed back to the input to sustain the output
  - B an intermediate frequency amplifier in a radio receiver
  - C a frequency modulator circuit
  - D not a circuit in electron
  - E an antenna.
- (x) Which of the following equations is true when the transistor is operating normally?
- A  $I_E = I_C + I_B$
  - B  $I_C = I_E + I_B$
  - C  $I_B = I_C + I_E$
  - D  $I_E = I_B - I_C$
  - E  $I_B = I_C$

#### SECTION B (30 marks)

Answer all questions in this section.

2. Define gain as applied to amplifiers.
3. Draw on the same axis, choosing suitable scales, typical characteristics for silicon and germanium diodes.
4. State three (3) uses of r.f. oscillators.
5. State three (3) advantages of using integrated circuits over discrete component circuits.
6. State three (3) ways in which radio waves travel.
7. Explain briefly the terms a.g.c. and a.f.c.
8. Explain with the help of a diagram the term "side frequencies" in A.M.
9. State two (2) ways of using a variable resistor.
10. What value of capacitance would give a resistance of  $50\ \Omega$  at 700 Hz?
11. Distinguish between choke and capacitor in operation.



**SECTION C (60 marks)**

Answer three (3) questions from this section.

12. (a) What is an image frequency?  
(b) How can the second-channel interference be minimized?  
(c) A superhet radio receiver has an intermediate frequency of 470 kHz and is tuned to 1065 kHz. Calculate the  
(i) Frequency of the local oscillator.  
(ii) Frequency of the image.
13. (a) Define the term feedback.  
(b) Draw a well-labelled block diagram just to show the feedback loop.  
(c) A wide-band amplifier has gain of (-1000) without feedback and (-20) with negative feedback. Find the  
(i) Value of  $\beta$ .  
(ii) Percentage reduced in gain with the gain without feedback falls by 40 percent.
14. (a) Name two (2) applications of a zener diode.  
(b) Draw a simple half wave rectifier with a reservoir capacitor and then draw its output waveform.  
(c) If zener diode has 500 mW with breakdown voltage of 5.1 V.  
(i) what will its maximum current be?  
(ii) find resistance R if the maximum voltage of 3.9 V is dropped across R.
15. Define the following terms used in T.V.  
(a) T.V. camera  
(b) Chroma  
(c) Phosphor  
(d) Field  
(e) Scanning.
16. (a) (i) What is alignment in radio receiver servicing?  
(ii) State three (3) tuneable sections during radio alignment.  
(b) Your radio receiver is completely dead (i.e. no sound at the output). Before taking any action for repair, what do you suspect to be the possible two (2) problems?