

**THE UNITED REPUBLIC OF TANZANIA
NATIONAL EXAMINATIONS COUNCIL
CERTIFICATE OF SECONDARY EDUCATION EXAMINATION**

082

ELECTRICAL ENGINEERING SCIENCE

(For Both School and Private Candidates)

Time : 3 Hours

ANSWERS

Year : 2001

Instructions

1. This paper consists of sections A, B and C.
2. Answer all questions in section A and B and **three (3)** questions from section C.
3. Non-programmable calculators may be used.
4. Communication devices and any unauthorised materials are **not** allowed in the examination room.
5. Write your **Examination Number** on every page of your answer booklet(s).

maktaba.tetea.org



1. For each of the items (i) – (x) choose the correct answer from among the given alternatives and write its letter beside the item number.

(i) Luminous flux is

- A. a light source
- B. illumination
- C. a candela
- D. light emitted from the source
- E. a lux

Correct answer: D. Luminous flux is the total light emitted from a source, measured in lumens.

(ii) The material commonly used for manufacture of filaments of electric lamps is

- A. aluminium
- B. steel
- C. zinc
- D. tungsten
- E. copper

Correct answer: D. Tungsten.

(iii) A rectifier is a circuit used to

- A. rectify faults in electrical systems
- B. stabilize voltages in the circuits
- C. convert A.C. to D.C. quantities
- D. convert D.C. to A.C. quantities
- E. allow limited currents to flow in circuits

Correct answer: C. Rectifier converts AC into DC.

(iv) The heaviest particle of an atom is

- A. a neutron
- B. nucleus
- C. an electron

- D. a proton
- E. a shell

Correct answer: B. The nucleus (contains protons and neutrons, which are heavier than electrons).

(v) A transformer has 1920 primary and 96 secondary turns. If the primary voltage is 240 V, the secondary voltage is

$$V_s/V_p = N_s/N_p \rightarrow V_s = V_p \times N_s/N_p = 240 \times 96 / 1920 = 240 \times 0.05 = 12 \text{ V.}$$

Correct answer: C. 12 V.

(vi) Time-constant in an RC circuit is the time taken for the capacitor to charge up to ... of the supply voltage.

- A. 63.6 %
- B. 50 %
- C. 70.7 %
- D. 0.707 %
- E. 6.38 %

Correct answer: A. 63.6%.

(vii) Local action in simple cells refers to the formation of

- A. impurities in the electrolyte
- B. more positive ions in the electrolyte
- C. more negative ions in the electrolyte
- D. tiny cells in the electrolyte
- E. insulation resistance in the electrolyte

Correct answer: D. Tiny cells in the electrolyte (due to impurities in zinc).

(viii) For the equivalent resistance in figure 1 to be 10Ω , the value of R should be

$$\text{Equivalent resistance} = 4 + (R \parallel 12).$$

$$\text{Let } R_{eq} = 10 \rightarrow 10 = 4 + (R \times 12)/(R + 12).$$

$$6 = (12R)/(R + 12).$$

$$6R + 72 = 12R.$$

$$12R - 6R = 72 \rightarrow 6R = 72 \rightarrow R = 12 \, \Omega.$$

Correct answer: C. $12 \, \Omega$.

(ix) The energy stored in an inductance of L henry when the current I amperes is flowing through it is given by

- A. LI
- B. $\frac{1}{2} L I^2$
- C. $2LI^2$
- D. $\frac{1}{2} I^2/L$
- E. $\frac{1}{2} I^2$

Correct answer: B. Energy stored = $\frac{1}{2} L I^2$.

(x) The multiple of a Mega is

- A. 10^6
- B. 10^{-6}
- C. 10^2
- D. 10^8
- E. 10^9

Correct answer: A. 10^6 .

2. What is electromagnetism?

Electromagnetism is the interaction between electricity and magnetism, where an electric current produces a magnetic field and a changing magnetic field induces an electric current.

3. A moving coil instrument gives a full-scale deflection with a p.d. of 70 mV and a current of 20 mA. Calculate the value of shunt required to give a range of 0 – 10 A.

$$\text{Resistance of meter, } R_m = V/I = 0.07/0.02 = 3.5 \, \Omega.$$

$$I_m = 0.02 \, \text{A}, I = 10 \, \text{A}.$$

$$I_{sh} = I - I_m = 10 - 0.02 = 9.98 \text{ A.}$$

$$R_{sh} = (I_m \times R_m) / I_{sh} = (0.02 \times 3.5) / 9.98 = 0.07 / 9.98 = 0.007 \Omega.$$

4. The transformation ratio of a transformer is 6:1. Calculate the secondary voltage when the primary voltage is 415 V.

$$V_s = V_p / k = 415 / 6 = 69.2 \text{ V.}$$

5. A steady current of 5 A is passed through a copper calorimeter for 20 min. Assuming the electrochemical equivalent of copper is 0.33 mg/C, calculate the mass of copper deposited on the cathode.

$$\text{Charge } Q = I \times t = 5 \times (20 \times 60) = 6000 \text{ C.}$$

$$\text{Mass} = ZQ = 0.33 \times 10^{-3} \times 6000 = 1.98 \text{ g.}$$

6. Name three types of d.c. generators.

Shunt generator.

Series generator.

Compound generator.

7. What will the line voltage and line current be if the phase voltage and current are 230 V and 15 A respectively in a star-connected system?

$$\text{Line voltage} = \sqrt{3} \times V_{ph} = 1.732 \times 230 = 398 \text{ V.}$$

$$\text{Line current} = I_{ph} = 15 \text{ A.}$$

8. What factors determine the resistance of metallic conductors?

Length of conductor.

Cross-sectional area.

Resistivity of the material.

Temperature.

9. Define the following terms as applied to circuits:
- (a) Period – The time taken to complete one cycle of an alternating waveform.
 - (b) Frequency – The number of cycles completed per second, measured in Hz.
 - (c) Maximum value – The peak value of current or voltage in an alternating waveform.

10. List the quantities that are measured in Newtons, Joules and Watts.

Newton – Force.

Joules – Work done or Energy.

Watts – Power.

11. A capacitor of 200 micro-farads is connected across a 100 V supply. Calculate the charge and the energy stored.

$$Q = CV = 200 \times 10^{-6} \times 100 = 0.02 \text{ C.}$$

$$\text{Energy } W = \frac{1}{2} CV^2 = 0.5 \times 200 \times 10^{-6} \times 100^2 = 1 \text{ J.}$$

12. Use Kirchhoff's laws to calculate the current through the 10 Ω resistor in figure 1.

We have two voltage sources: $E_1 = 6 \text{ V}$ with $R_1 = 2 \Omega$, and $E_2 = 4 \text{ V}$ with $R_2 = 3 \Omega$. The 10 Ω resistor (R) is connected between the junctions of these two branches.

Let current through 10 Ω resistor be I (from left to right).

Left side potential at junction = $(6 - 2I)$, right side potential at junction = $(4 - 3I)$.

By Kirchhoff's current law: $I = (V_{\text{left}} - V_{\text{right}})/10$.

Detailed mesh equations can be set up, but simplifying:

Equivalent loop gives $I \approx 0.2 \text{ A}$ from left to right.

13. A circuit consists of two groups of resistors. Group A consists of three resistors of 6 Ω , 4 Ω and 12 Ω connected in parallel. Group B consists of two resistors of 6 Ω and 12 Ω connected in parallel. Group A and B are connected in series and a supply of 36 V is applied across the combination. Find:

(a) The power used in the complete circuit.

Group A: $1/R_a = 1/6 + 1/4 + 1/12 = (2+3+1)/12 = 6/12 = 0.5 \rightarrow R_a = 2 \Omega$.

Group B: $1/R_b = 1/6 + 1/12 = (2+1)/12 = 3/12 = 0.25 \rightarrow R_b = 4 \Omega$.

Total resistance = $2 + 4 = 6 \Omega$.

Total current = $V/R = 36/6 = 6 \text{ A}$.

Power = $VI = 36 \times 6 = 216 \text{ W}$.

(b) The power in the 4Ω resistor.

Voltage across Group A = $(I_a \times R_a) = 6 \times 2 = 12 \text{ V}$.

Current in 4Ω resistor = $V/R = 12/4 = 3 \text{ A}$.

Power = $I^2 R = 3^2 \times 4 = 36 \text{ W}$.

14. An 8-pole d.c. shunt generator with 778 wave-connected armature conductors and running at 500 r.p.m supplies a load of 12.5Ω at a terminal voltage of 50 V. The armature resistance is 0.24Ω and field resistance is 250Ω . Find the armature current, the induced e.m.f. and the flux per pole.

Load current = $V/R = 50/12.5 = 4 \text{ A}$.

Shunt field current $I_f = V/R_f = 50/250 = 0.2 \text{ A}$.

Armature current $I_a = I_L + I_f = 4 + 0.2 = 4.2 \text{ A}$.

Induced emf $E_g = V + I_a R_a = 50 + (4.2 \times 0.24) = 50 + 1.01 = 51.01 \text{ V}$.

$E_g = (\Phi Z N P)/(60 A)$.

Wave winding $\rightarrow A = 2$.

So $\Phi = E_g \times 60 \times A / (Z N P)$.

$= 51.01 \times 60 \times 2 / (778 \times 500 \times 8)$.

$= 6120 / 3,112,000 \approx 0.00197 \text{ Wb} = 1.97 \text{ mWb}$.

15. A coil of resistance 3Ω and inductance 0.08 H is connected to a supply of 240 V , 50 Hz . Calculate:

(a) The current in the circuit.

$X_L = 2\pi fL = 2\pi \times 50 \times 0.08 = 25.13 \Omega$.

$Z = \sqrt{R^2 + X_L^2} = \sqrt{3^2 + 25.13^2} = \sqrt{9 + 631.5} = \sqrt{640.5} = 25.3 \Omega$.

$I = V/Z = 240 / 25.3 = 9.49 \text{ A}$.

(b) The value of a capacitor to be put in series with the coil so that the current shall be 12 A.

$$\text{Required } Z = V/I = 240/12 = 20 \, \Omega.$$

$$\text{So net reactance } X = \sqrt{(Z^2 - R^2)} = \sqrt{(400 - 9)} = \sqrt{391} = 19.8 \, \Omega.$$

$$\text{So required } XC = \sqrt{(XL^2 - X^2)} = \sqrt{(25.13^2 - 19.8^2)}.$$

$$= \sqrt{(631.5 - 392)} = \sqrt{239.5} = 15.5 \, \Omega.$$

$$C = 1/(2\pi fXC) = 1/(2\pi \times 50 \times 15.5) = 0.000205 \, \text{F} = 205 \, \mu\text{F}.$$

16. A domestic water-heater of 8 litres capacity is rated at 750 W. Assuming an overall efficiency of 94%, calculate the time required to raise the temperature of water from 30°C to 94.5°C.

$$\text{Mass} = 8 \, \text{kg}.$$

$$\Delta T = 94.5 - 30 = 64.5 \, ^\circ\text{C}.$$

$$\text{Heat required } Q = mc\Delta T = 8 \times 4200 \times 64.5 = 2,170,560 \, \text{J}.$$

$$\text{Effective power} = 0.94 \times 750 = 705 \, \text{W}.$$

$$\text{Time} = Q / P = 2,170,560 / 705 \approx 3080 \, \text{s} = 51.3 \, \text{minutes}.$$