

**THE UNITED REPUBLIC OF TANZANIA  
NATIONAL EXAMINATIONS COUNCIL  
CERTIFICATE OF SECONDARY EDUCATION EXAMINATION**

**031/2B**

**PHYSICS 2B  
ACTUAL PRACTICAL B  
(For Both School and Private Candidates)**

**Time: 2:30 Hours**

**Tuesday, 17<sup>th</sup> November 2015 a.m.**

---

**Instructions**

1. This paper consists of **two (2)** questions. Answer **all** the questions.
2. Calculations should be clearly shown.
3. Marks for questions are indicated at the end of each question.
4. Calculators and cellular phones are **not** allowed in the examination room.
5. Write your **Examination Number** on every page of your answer booklet(s).
6. The following information may be useful:  
 $\pi = 3.14$ .

1. The aim of this experiment is to determine the spiral constant,  $K$ , by using a spiral spring.
- (a) Clamp the given spring provided and a meter rule as shown in Figure 1.


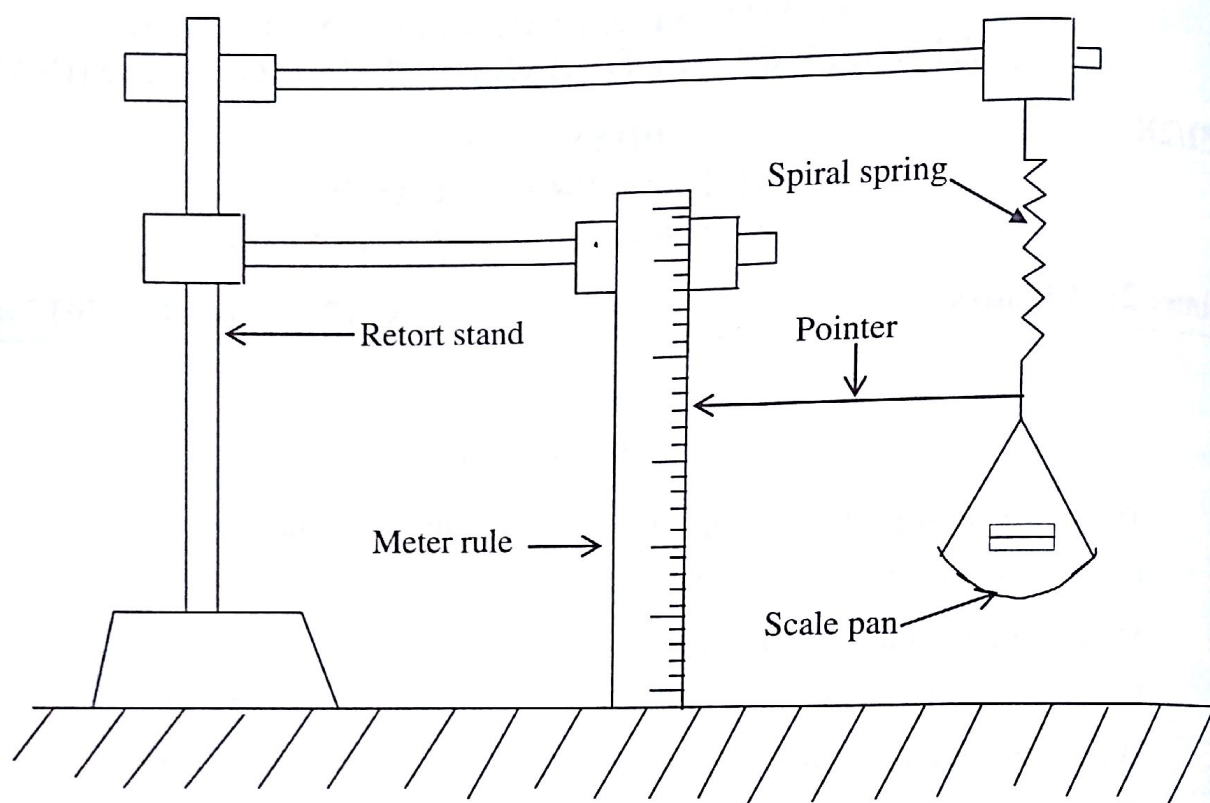


Figure 1

- (b) Read and record the position of the pointer on the meter rule before placing the mass on the scale pan.
- (c) Place a mass,  $m$ , equal to 100g on the scale pan and record the new position of the pointer on the meter rule.
- (d) Find the extension of the spring,  $e$ , in meters.
- (e) Remove the meter rule.
- (f) Pull the scale pan downwards through a small distance and release it.
- (g) Measure and record the time for twenty (20) oscillations. Find the time  $T$ , for one oscillation.
- (h) Repeat the procedures 1 (f) and (g) for values of  $m$  equal to 200g, 300g, 400g and 500g.
- (i) Tabulate your results.
- (j) Plot a graph of  $T^2$  against  $m$ .
- (k) Find the slope  $S$  of the graph.
- (l) Use the relation  $T = 2\pi\sqrt{\frac{m}{K}}$  to calculate the value of the spring constant  $K$ .
- (m) Suggest any two sources of errors and one precaution taken in the experiment.
- (25 marks)

2.

The aim of this experiment is to determine the internal resistance,  $r$ , of the cell provided.

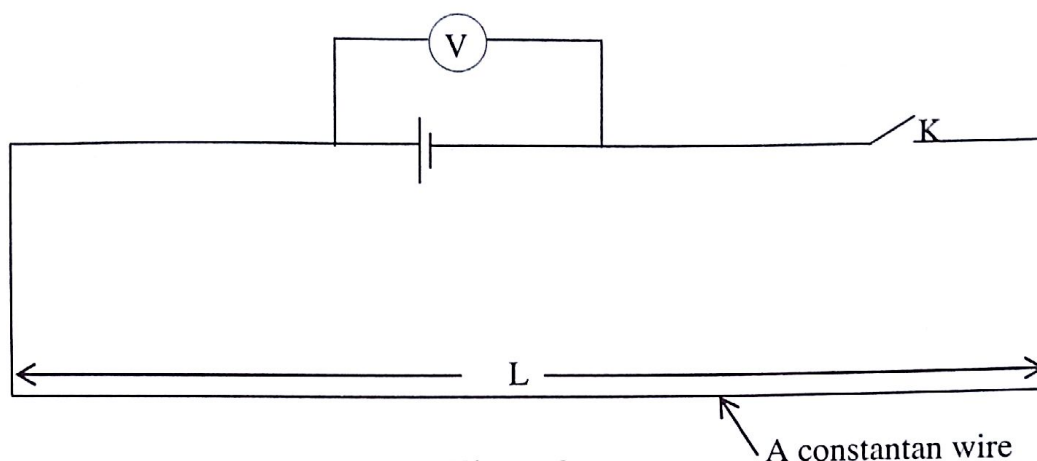

**Figure 2**

- (a) Connect the circuit as shown in the Figure 2.
- (b) Adjust the distance  $L$  to 20 cm.
- (c) Close the switch  $K$ .
- (d) Read and record the reading of the voltmeter  $V$ .
- (e) Repeat the procedures (b) to (d) for  $L = 30$  cm, 40cm, 50cm and 60cm.
- (f) Tabulate your results including values of  $\frac{1}{V}$  and  $\frac{1}{L}$ .
- (g) Plot a graph of  $\frac{1}{V}$  against  $\frac{1}{L}$ .
- (h) Find the slope,  $s$ , of the graph.
- (i) Read the intercept of  $\frac{1}{V}$  axis.
- (j) Calculate the value of the reciprocal of  $\frac{1}{V}$  intercept.
- (k) What does the value of the reciprocal of the intercept of  $\frac{1}{V}$  physically represent?
- (l) Calculate the internal resistance  $r$  of the cell from the relation  $r = 0.0795(V\Omega/\text{cm}) \times \text{slope}(s)$ .
- (m) List down two possible sources of errors and two precautions to be taken into account.

**(25 marks)**