

THE UNITED REPUBLIC OF TANZANIA
NATIONAL EXAMINATIONS COUNCIL OF TANZANIA
CERTIFICATE OF SECONDARY EDUCATION EXAMINATION

031/2B

PHYSICS 2B

(ACTUAL PRACTICAL B)


(For Both School and Private candidates)

Time: 2:30 Hours


Year: 2022

Instructions

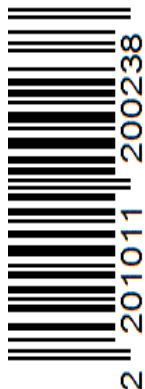1. This paper consists of **two (2)** questions.
2. Answer **all** questions.
3. Each question carries twenty **five (25)** marks.
4. All writing must be in **blue** or **black** ink **except** drawing which must be in pencil.
5. Cellular phones, and any unauthorized materials are **not** allowed in the examination room.
6. Write your **Examination Number** on every page of your answer booklet (s)



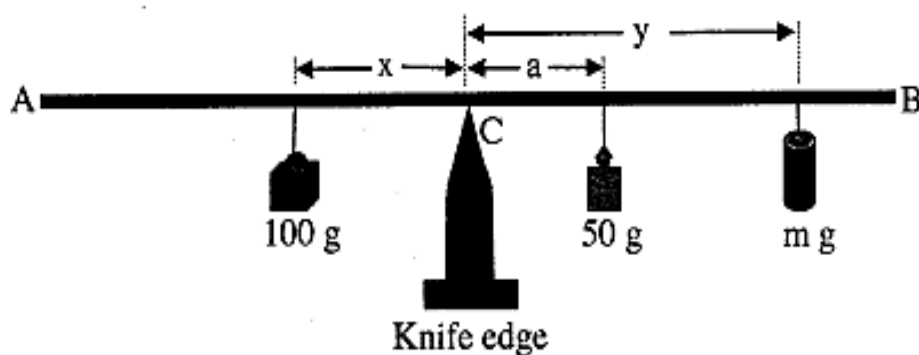
1. You are provided with unknown mass “m”, a knife edge, 50 g mass, 100 g mass, and a metre rule. Perform experiment through the following procedures:
- (a) Find and mark the centre of gravity **C** of the metre rule **AB** by balancing it freely on a knife edge.
 - (b) Place a metre rule on a knife edge at its centre of gravity **C**.
 - (c) Suspend the 100 g mass at point $x=10$ cm from the centre of gravity of a metre rule. Suspend 50 g mass at distance $a=5$ cm from **C** on the other side of **C**.
 - (d) Suspend the mass m to the side of 50 g mass and adjust it until the metre rule balances horizontally as shown in the following Figure.



- (e) Repeat the procedure in 1 (d) when $x = 15$ cm, 25 cm and 30 cm. Find the corresponding value of y (cm) in each experiment. Answer the following questions:
 - (i) Tabulate the results of x (cm) and y (cm).
 - (ii) Plot a graph of x (cm) against y (cm).
 - (iii) Calculate the slope of the graph.
 - (iv) Formulate the equation of the graph.
 - (v) Determine the unknown mass m .

2. Determine the e.m.f of the cell and the resistance of a given piece of wire through the following procedures:

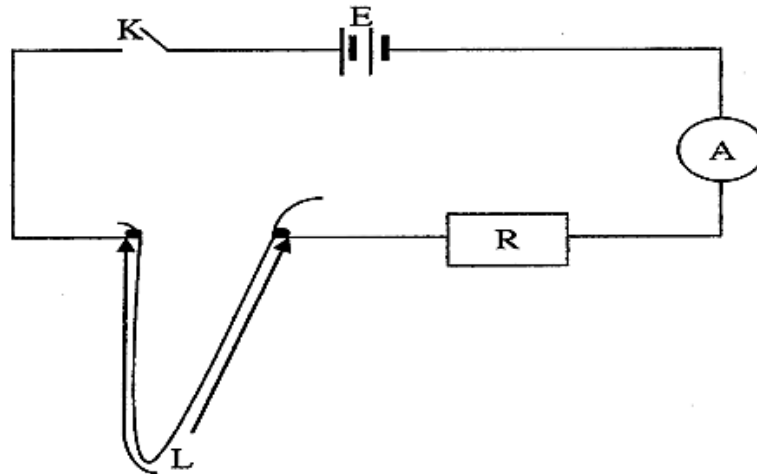- (a) Connect the circuit diagram as shown below in which E is a battery, K is a key, L is the length of the wire, R is the resistance box and A is an ammeter.



- (b) With $L = 12 \text{ cm}$ and R set at 1Ω , record the ammeter reading I (A).
- (c) Without altering the value of L , repeat the procedure in 2 (b) with $R = 2 \Omega, 3 \Omega, 4 \Omega$ and 5Ω . Record the corresponding values of ammeter reading in each case.
- (i) Tabulate the results of R , I and $\frac{1}{I}$.
- (ii) Plot a graph of $\frac{1}{I}$ against R .
- (iii) Calculate the slope S of the graph.
- (iv) Find the value of I for which $R = 0.91$
- (v) Determine the e.m.f and resistance of the wire L given that, the internal resistance of the cell was 1.0Ω . Show clearly how to arrive to the answers.