

**THE UNITED REPUBLIC OF TANZANIA  
NATIONAL EXAMINATIONS COUNCIL  
CERTIFICATE OF SECONDARY EDUCATION EXAMINATION**

**031/2B**

**PHYSICS 2B**

(For Both School and Private Candidates)

**Time : 3 Hours**

**ANSWERS**

**Year : 2024**

**Instructions**

1. This paper consists of sections A, B and C.
2. Answer all questions in section A and B and **one (1)** question from section C.
3. Non-programmable calculators may be used.
4. Communication devices and any unauthorised materials are **not** allowed in the examination room.
5. Write your **Examination Number** on every page of your answer booklet(s).

maktaba.tetea.org



**1. You are required to determine the mass  $m$  of a given solid body.**

(a) & (b) The setup is already described: pivot metre rule at midpoint, balance with 50 g at distance  $a$  and solid body  $m$  at distance  $b$ .

The principle of moments applies:

$$50 \times a = m \times b$$

Therefore,


$$m = (50 \times a) / b$$

(c) Suppose the following observations were obtained:

<b>a (cm)</b>	<b>b (cm)</b>
20	40
25	50
30	60
35	70
40	80

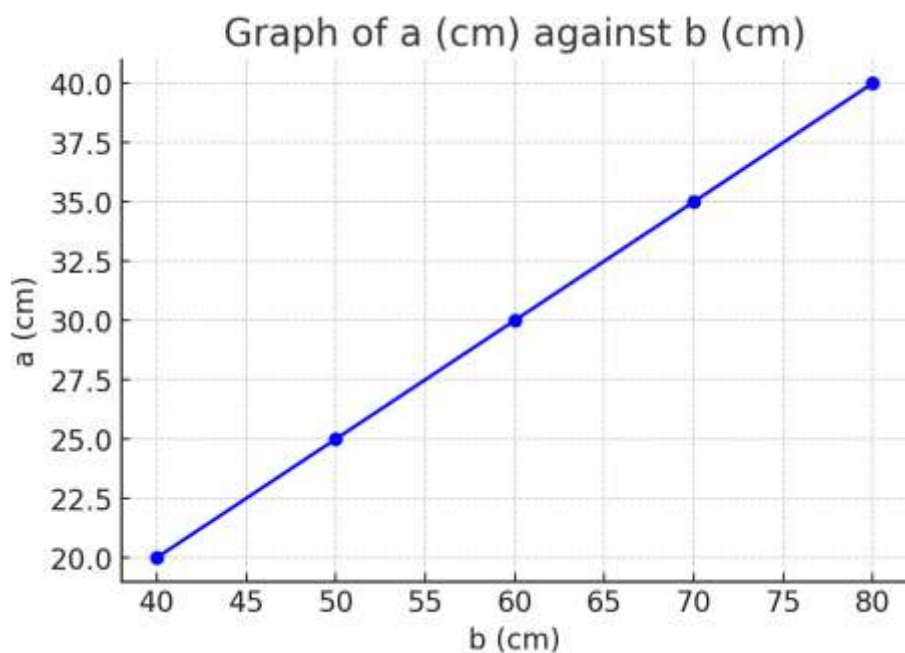**(ii) Graph of  $a$  against  $b$**

When plotted, the graph is a straight line passing through the origin.



**(iii) Nature of Graph**

The graph is linear, showing that  $a \propto b$ .

**(iv) Slope of the graph**

$$\text{Slope} = \Delta a / \Delta b = (40 - 20) / (80 - 40) = 20 / 40 = 0.5$$

**(v) Relative density of metre rule**

If the metre rule balanced at midpoint, the mass distribution is uniform, hence relative density  $\approx 1$  compared to water.

**(vi) Mass of the given body m**

From the relation  $m = (50 \times a) / b$ ,

Using any pair e.g.  $a = 20$ ,  $b = 40$ :

$$m = (50 \times 20) / 40 = 25 \text{ g}$$

Thus the mass of the given body is **25 g**.

**2. You have been provided with electrical apparatus to determine an unknown resistance  $R$ .**


**(a) Circuit diagram**

- Ammeter in series with cell, key, variable resistor  $R_h$ , and resistor  $R$ .
- Voltmeter connected in parallel across  $R$ .

**(b) & (c) Suppose the following readings were recorded:**

Current $I$ (A)	Voltage $V$ (V)
0.1	0.5
0.2	1.0
0.3	1.5
0.4	2.0
0.5	2.5

**(ii) Graph of  $V$  against  $I$**

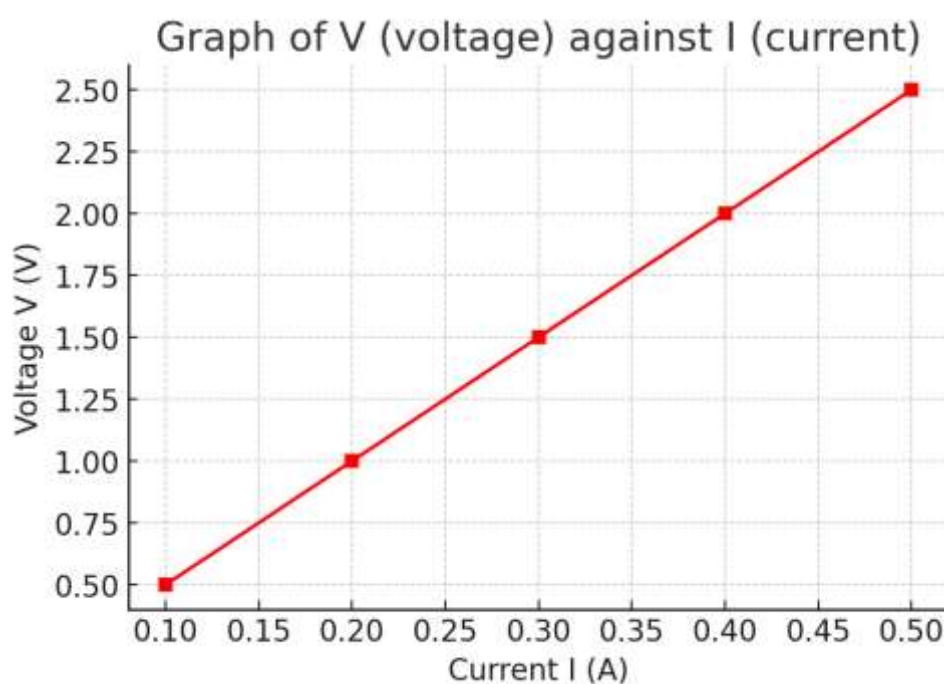

**(iii) Nature of Graph**

It is linear, confirming Ohm's Law ( $V \propto I$ ).

**(iv) Slope of Graph**

$$\text{Slope} = \Delta V / \Delta I = (2.5 - 0.5) / (0.5 - 0.1) = 2.0 / 0.4 = 5.0$$

**(v) Unknown resistance R**

$$R = \text{slope} = 5 \, \Omega$$

**(vi) Why high currents are unsuitable**

High currents may overheat R, damage the apparatus, or alter resistance due to heating effects.

**(vii) How to minimize error when calculating R**

Take multiple readings of V and I, plot a best-fit line, and determine R from the slope instead of a single reading.